

## ENR 325 Assignment #4


Due: 10/2/25 10:00 pm
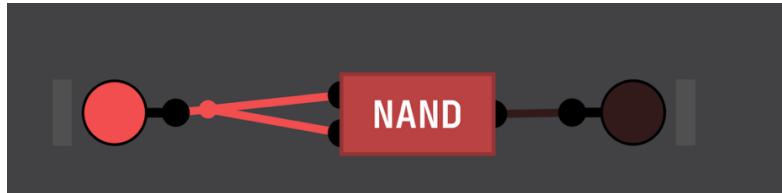
### Task 1: Let's play a bit more on the Digital Logic Sim

At the start of a new project, we only have NAND gate available:



But we can build other gates with NAND, here's the NOT (inverter) for example:




And we can save it as NOT gate:



So now your task is to build all the other gates and save them into your current project:  
AND, OR, NOT, NOR and XOR

**Send me a screen capture of all the gates you built with NAND.** (or NAND + other gates, for example, an AND gate can be built with NAND and NOT).

Here's a helper file below:

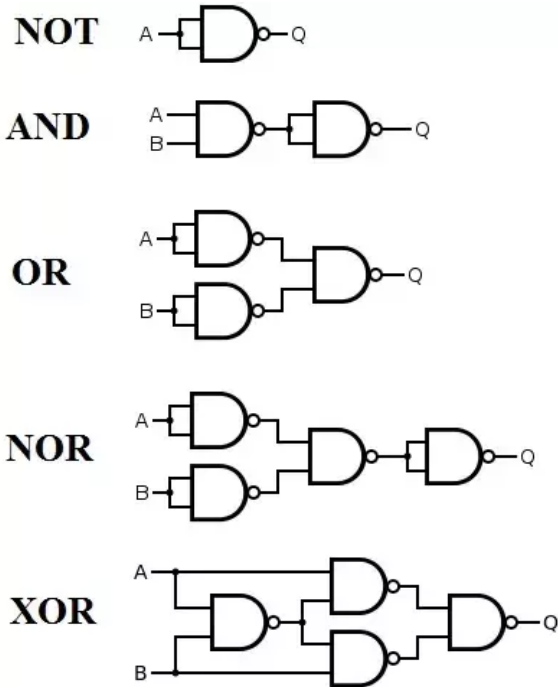


**Task 2: build a Hamming (7,4) in the digital logic sim.**

We talked about even parity check can be down with one logic function XOR.

So now your task is to build a Hamming (7,4) with the XOR gate you built in task one.

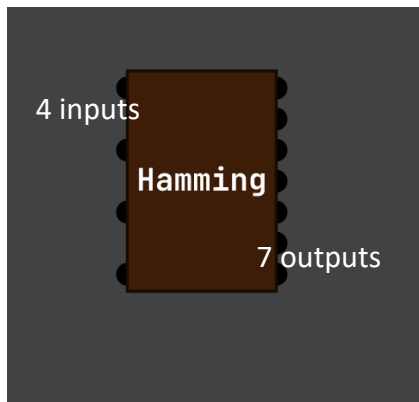**Send me a screenshot of the Hamming encoder chip you built:**



**You have to show what is under the hood.** If you want to do extended Hamming (plus total parity check), even better!

For detailed instruction, search Ben Eater's Hamming code video on YouTube. But I suggest you try to work it out on your own first.